

-
1. For the network of Fig. 1:
 - (a) Determine Z_i and Z_o .
 - (b) Find A_v and A_i .
 - (c) Repeat part (a) with $r_o = 20 \text{ k}\Omega$.
 - (d) Repeat part (b) with $r_o = 20 \text{ k}\Omega$.
-
2. (**Report**) For the network of Fig. 2, determine V_{CC} for a voltage gain of $A_v = -200$.
-
3. For the network of Fig. 3:
 - (a) Determine r_e .
 - (b) Calculate Z_i and Z_o .
 - (c) Find A_v and A_i .
 - (d) Repeat parts (b) and (c) with $r_o = 25 \text{ k}\Omega$.
-
4. For the network of Fig. 4:
 - (a) Determine r_e .
 - (b) Find Z_i and Z_o .
 - (c) Calculate A_v and A_i .
 - (d) Repeat parts (b) and (c) with $r_o = 20 \text{ k}\Omega$.
-
5. (**Report**) For the network of Fig. 5, determine R_E and R_B if $A_v = -10$ and $r_e = 3.8 \text{ }\Omega$. Assume that $Z_b = \beta R_E$.
-
6. For the network of Fig. 6:
 - (a) Determine r_e .
 - (b) Find Z_i and A_v .
 - (c) Calculate A_i .
-
7. (**Report**) For the network of Fig. 7:
 - (a) Determine Z_i and Z_o .
 - (b) Find A_v .
 - (c) Calculate V_o if $V_i = 1 \text{ mV}$.
-
8. For the network of Fig. 8, determine A_v and A_i .
-
9. For the collector FB configuration of Fig. 9:
 - (a) Determine r_e .
 - (b) Find Z_i and Z_o .

(c) Calculate A_v and A_i .

10. **(Report)** Given $r_e=10$, $\beta= 200$, $A_v= -160$, and $A_i= 19$ for the network of Fig. 10, determine R_C , R_F , and V_{CC} .

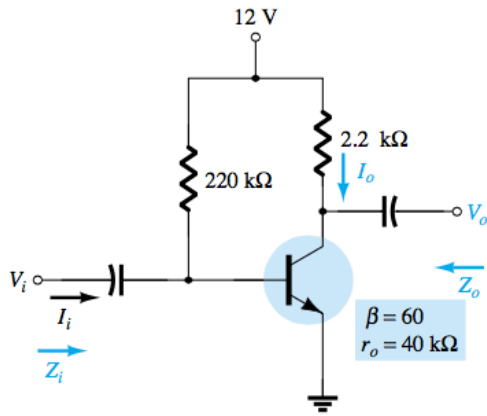


Fig.1

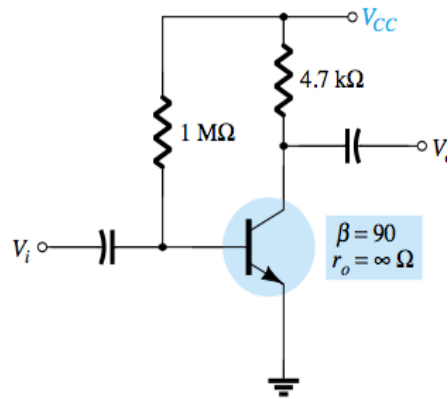


Fig.2

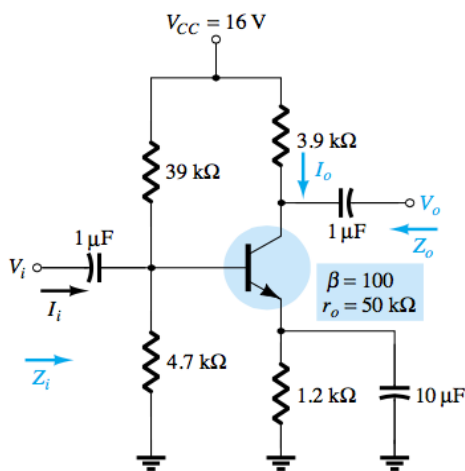


Fig.3

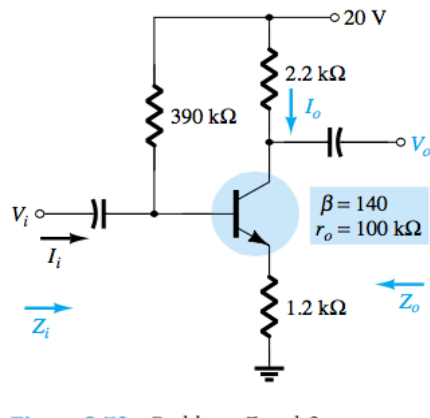


Fig.4

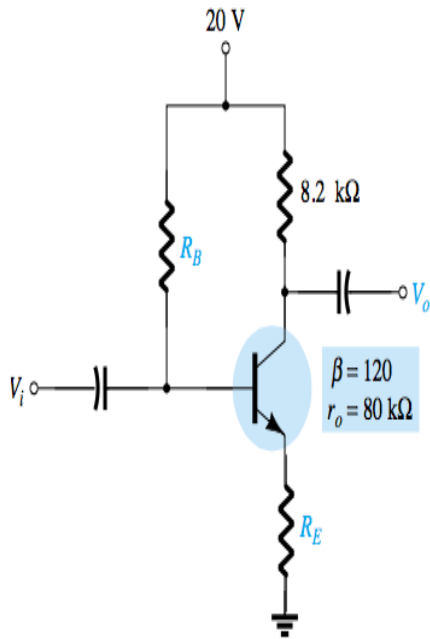


Fig.5

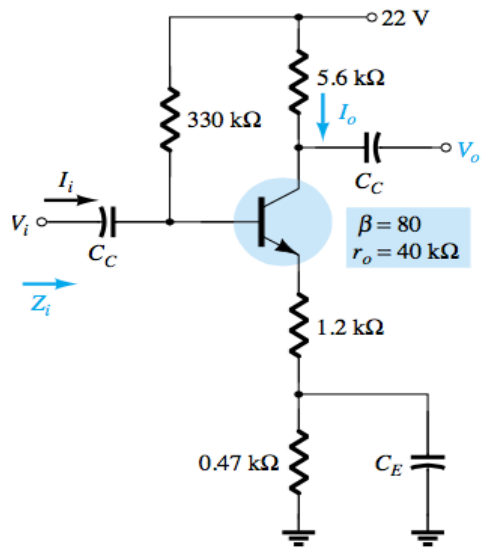


Fig.6

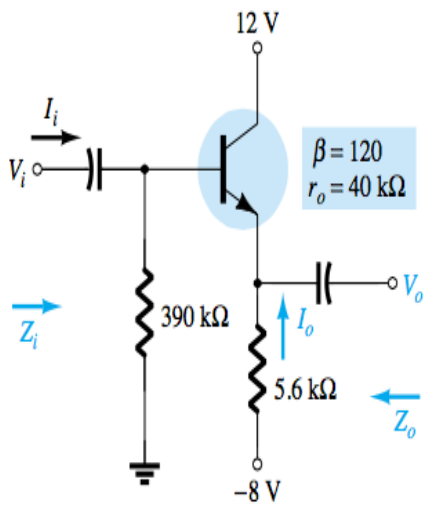


Fig.7

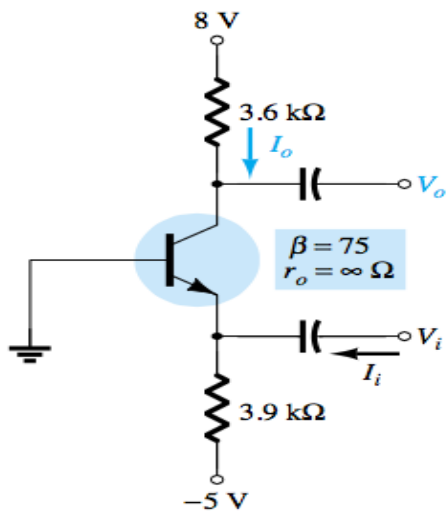


Fig.8

Fig. 8.78:

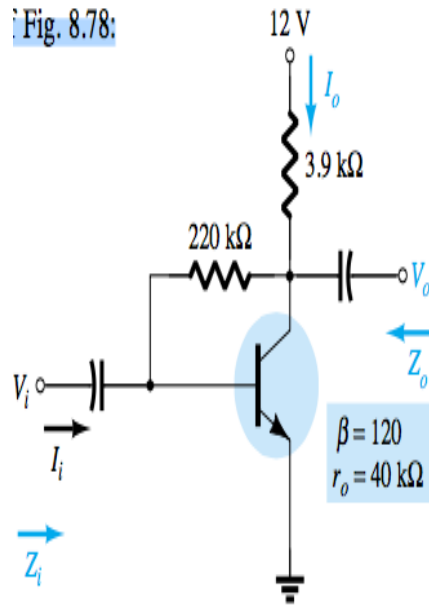


Fig.9

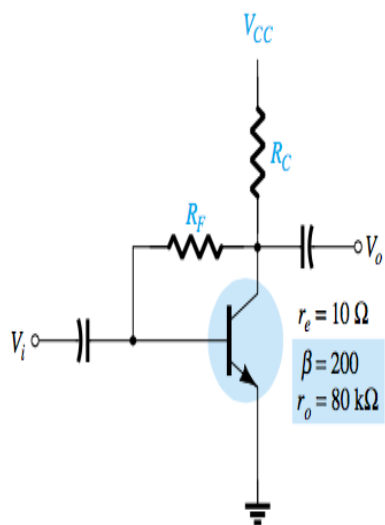


Fig.10